
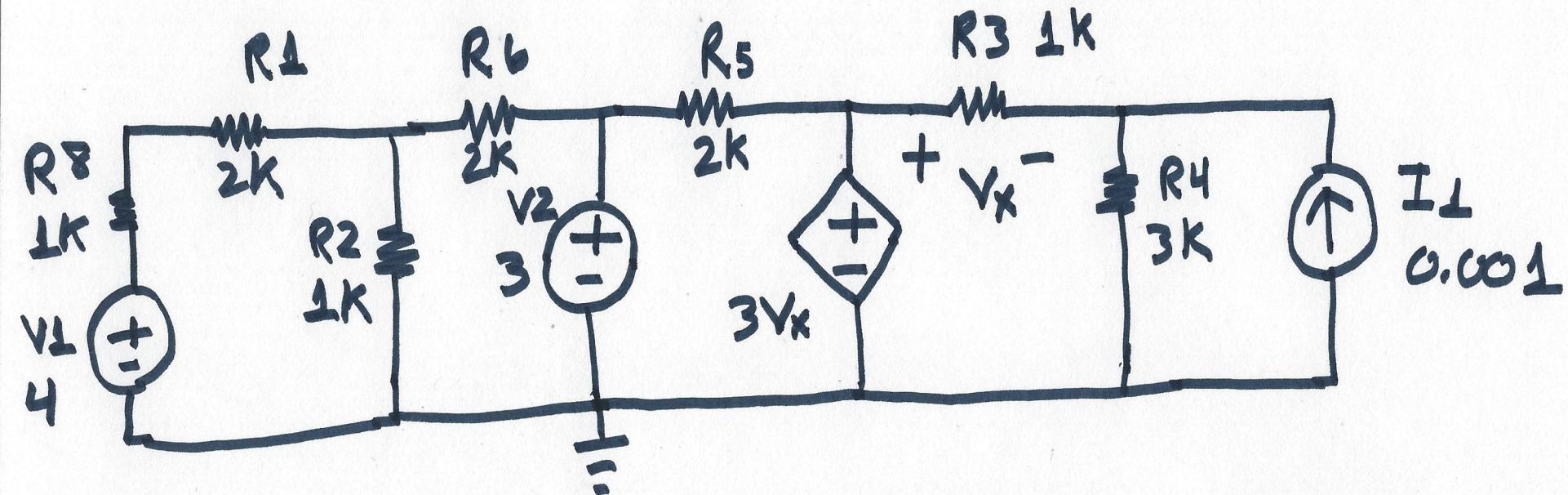

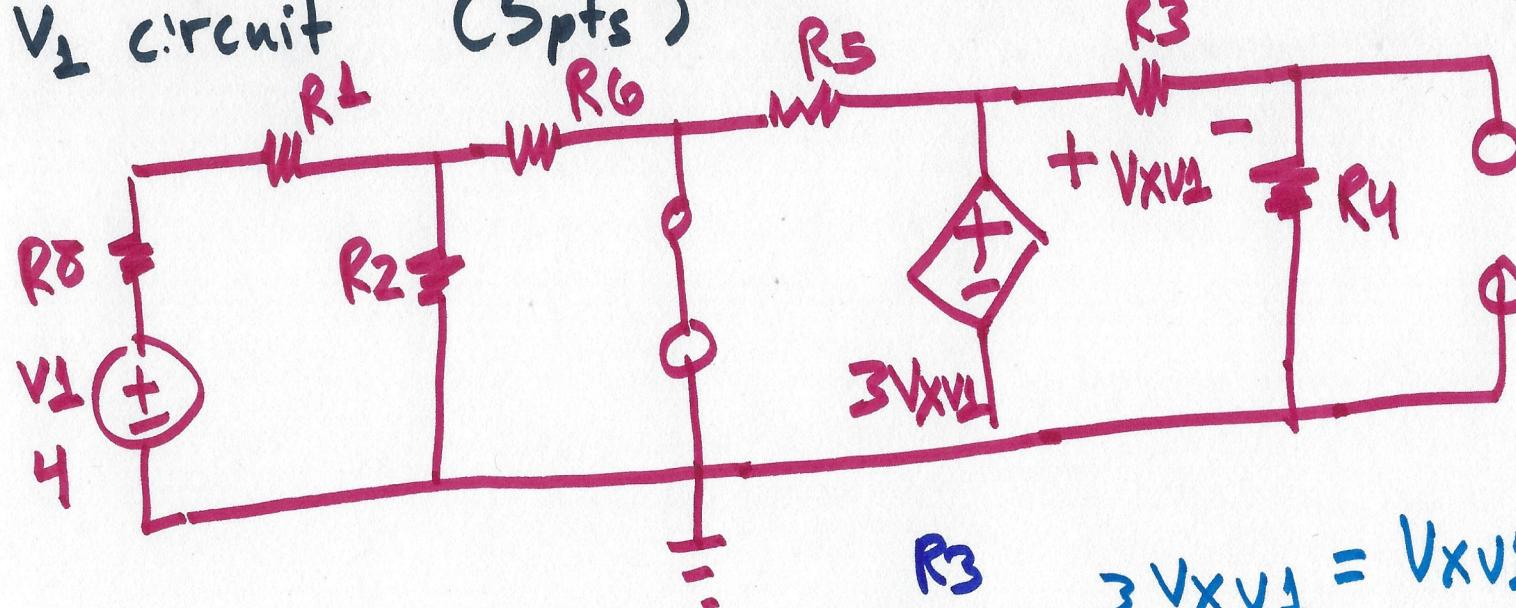
#3) Circuit Analysis II - Superposition/Dependent Sources (16 points)



Use Superposition to determine the Voltage V_x in the above circuit. Include a schematic of the circuit associated with each source.

V_L circuit (5pts)




$$\frac{R_4}{R_3 + R_4} V_{xv1}$$



$$3V_{xv1} = V_{xv1} + V_{R4}$$

$$R_4 = \frac{3}{4} V_{xv1}$$

$$V_{xv1} = 0$$

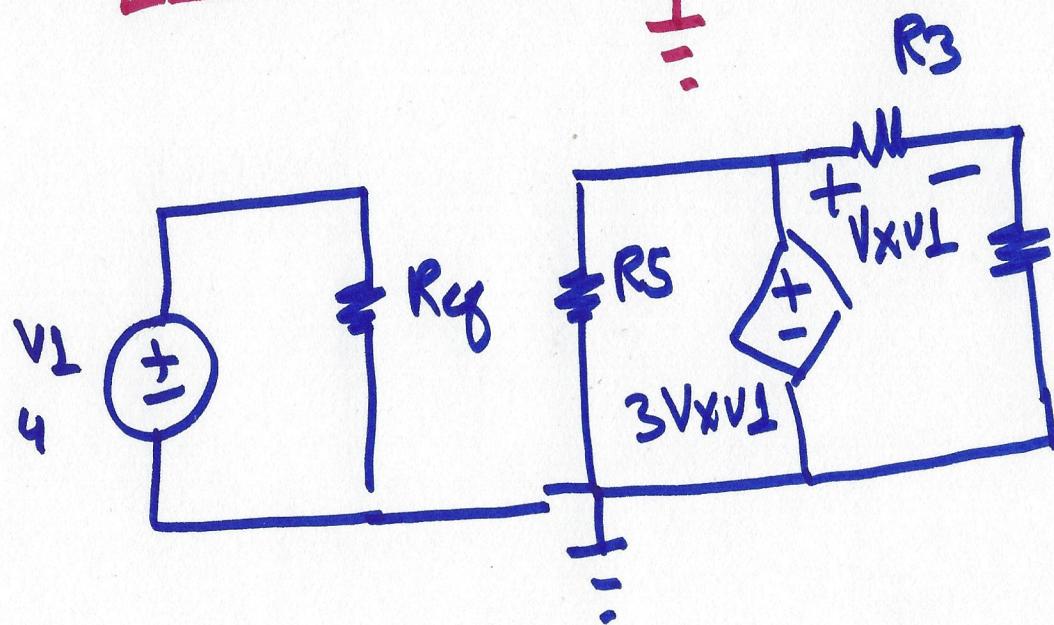

V_2 circuit (5pts)

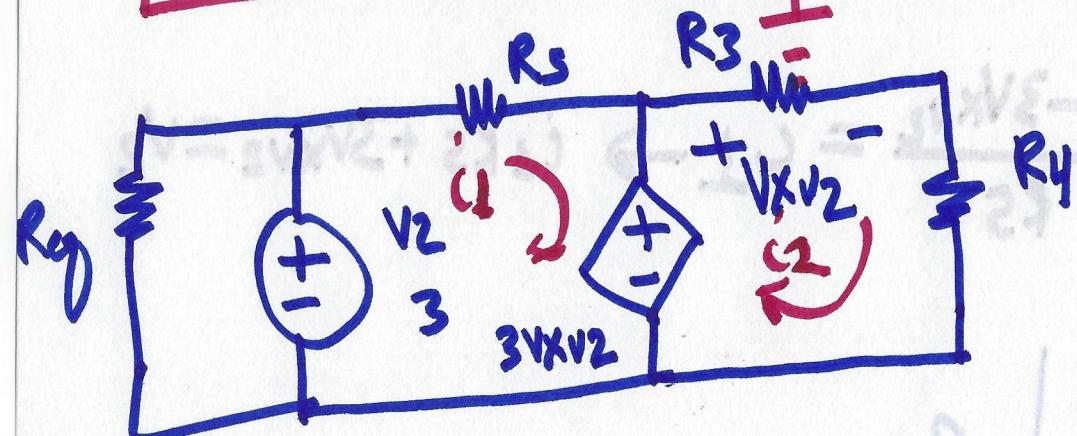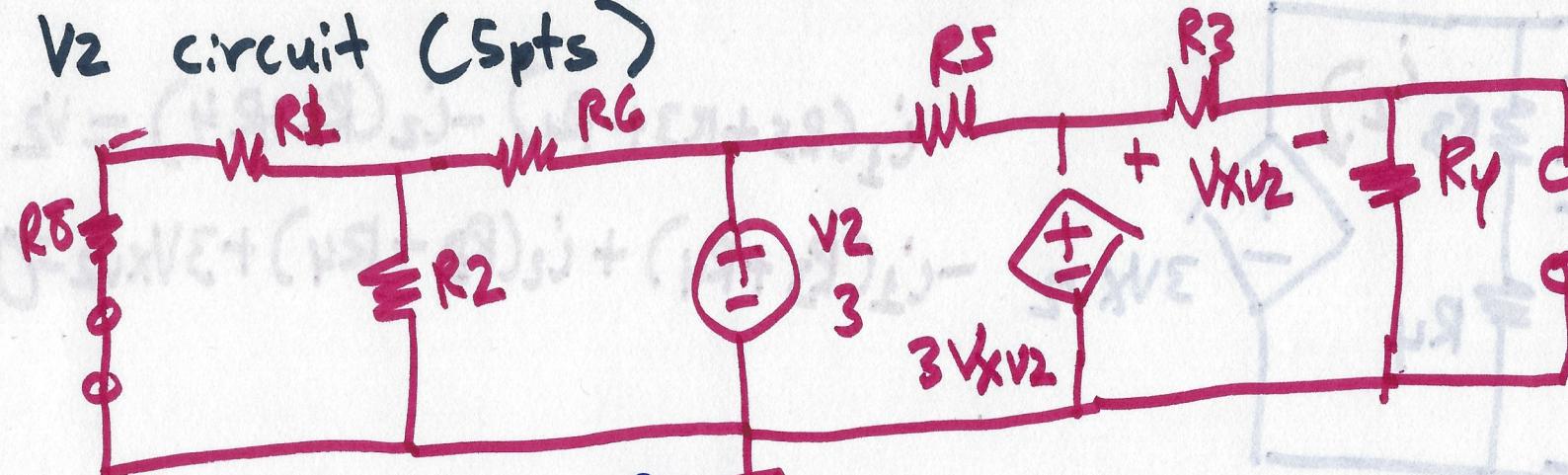

$$i_1 R_5 + 3V_{xv2} = V_2 \quad (1)$$

$$(R_3 + R_4)i_2 - 3V_{xv2} = 0 \quad (2)$$


$$i_2 R_3 = 3V_{xv2}$$

$$\rightarrow i_2 R_3 - 3V_{xv2} = 0 \quad (3)$$

$$i_1 = 0.0015$$

$$i_2 = 0$$

$$V_{xv2} = 0$$

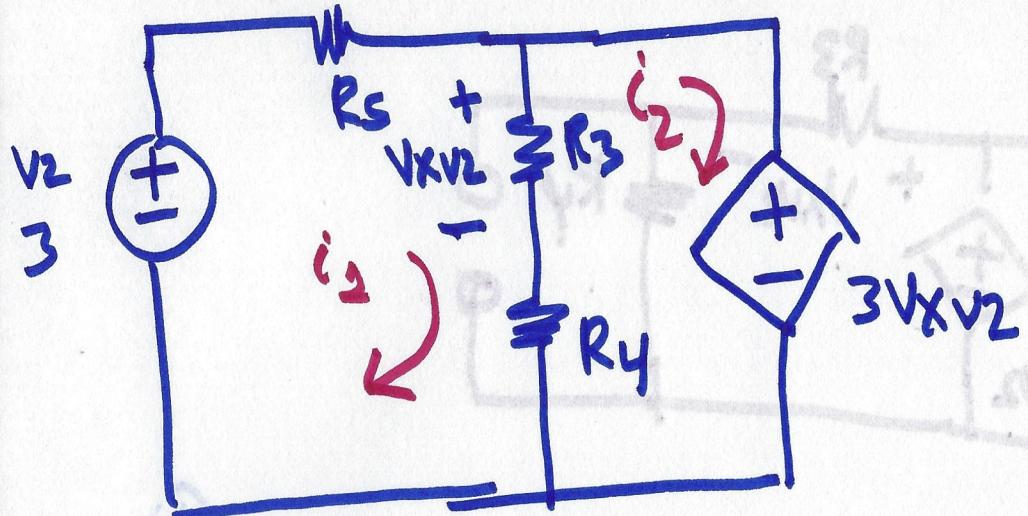

$$i_1(R_5 + R_3 + R_4) - i_2(R_3 + R_4) = V_2$$


$$-i_1(R_3 + R_4) + i_2(R_3 + R_4) + 3Vxv_2 = 0$$

$$\frac{V_2 - 3Vxv_2}{R_5} = i_1 \rightarrow i_1 R_5 + 3Vxv_2 = V_2$$

$$i_1 = 0.0015$$

$$i_2 = 0.0015$$


$$Vxv_2 = 0$$

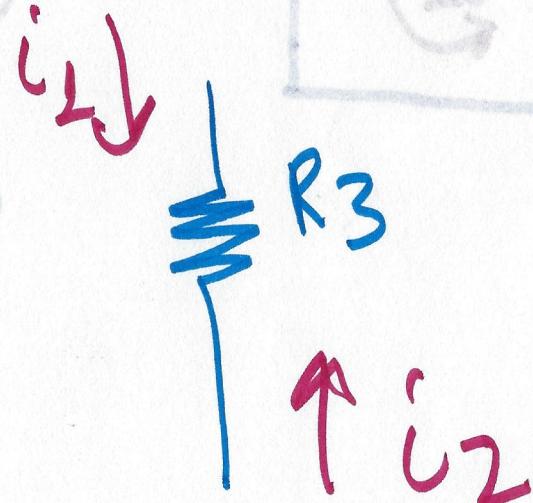

$$V_3 = 0$$


$$\boxed{Vxv_2 = 0}$$

I_1 circuit (5pts)

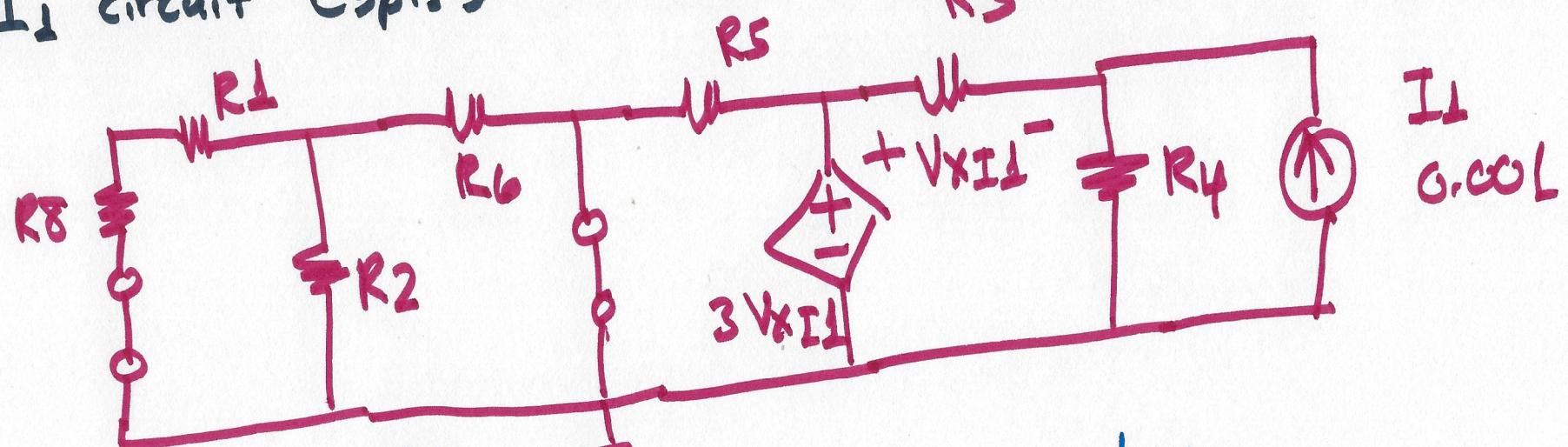

KCL

$$I_1 + \frac{V_x I_1}{R_3} = i_4$$

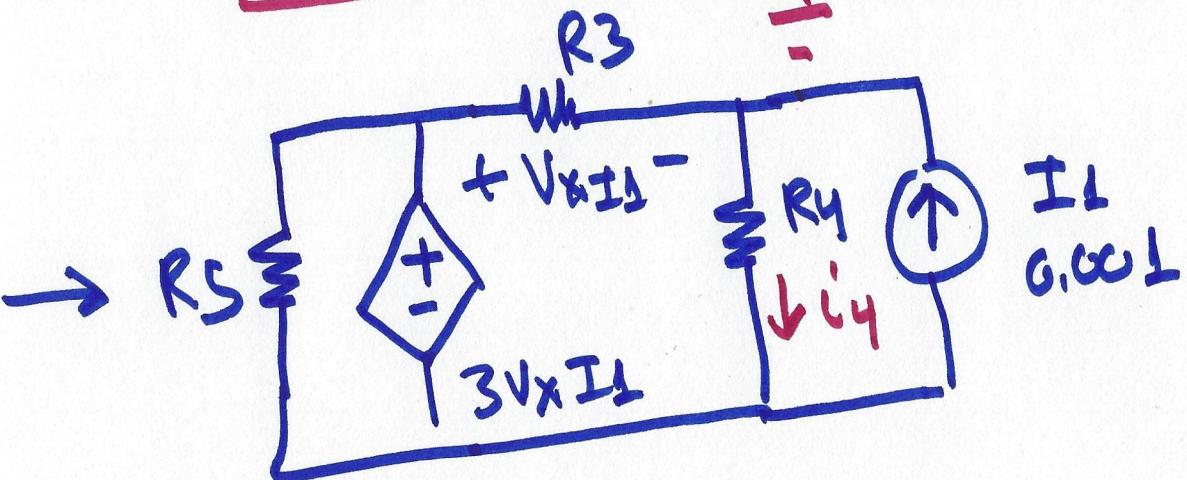

$$\text{kvl: } 3V_x I_1 = V_x I_1 + i_4 R_4 = V_x I_1 + R_4 \left[I_1 + \frac{V_x I_1}{R_3} \right]$$

$$2V_x I_1 = R_4 \left[I_1 + \frac{V_x I_1}{R_3} \right] \left(3 - \left(1 + \frac{R_4}{R_3} \right) \right) = -3V$$

$$V_x I_1 = -3V$$

Voltage across V_x (include polarity) ($\perp pt$)

$$V_x = V_x v_1 + V_x v_2 + V_x I_1$$
$$= -3V$$